

Low-noise, low-cost cassette deck

For some years the author had contemplated the possibilities for the provision of music of reasonable technical quality, by way of headphones, while away from home on camping holidays – which were normally taken in scenically attractive but physically remote parts of the countryside. Of the available alternatives, the use of previously recorded tape cassettes seemed the most satisfactory, but it is unlikely that further action would have been taken on this matter but for the current availability at an attractive price of good-quality cassette mechanisms made under Staar patents by Garrard and Goldring-Lenco.

It must be explained, at the outset, that the intention was not to provide an instrument which would equal or exceed that of expensive and carefully engineered “transcription” cassette recorders, but rather to evolve a straightforward and relatively inexpensive circuit arrangement which would nevertheless provide a standard of performance which would be acceptable in the context of existing, high quality, audio equipment. In the event, the performance of the prototype has substantially exceeded expectations, and has led to a major revision of the author’s opinion of the performance obtainable from this medium.

In particular, it would appear that, with good system design and appropriate attention paid to recording and bias levels in a direct recording made

High-quality design for mains / battery use

by J. L. Linsley Hood

from a good quality l.p. disc onto a reasonable quality ferric-oxide cassette tape, the major component of noise on replay is likely to be the surface noise on the original disc. Also, the differences between the source material and the cassette transcript can be sufficiently small that they are not readily apparent, even on A-B comparison.

Basic circuit

The general layout of the system adopted is shown in Fig. 1. The d.c. power supply unit has two outputs – one of about 12-14V at 200-400mA to feed the d.c. drive motor which operates the cassette feed, and which has its own speed control system incorporated by the manufacturers, in the case of the Garrard CT4 used in the prototype – and one having a well-smoothed and electronically stabilized output preset to a nominal 13.5V, which feeds either the replay or record amplifiers. Between

these two lines there are two change-over switches, to the centre point of which can be connected a 12-14V d.c. supply, so that the system can also be operated from batteries.

The changeover switch in the amplifier supply line is a small microswitch, not supplied with the cassette mechanism but operated by a protruding tag on the side of the record push button on the mechanism. To make a recording, this is depressed before the cassette is inserted, when a mechanical interlock retains the button in the inward position. When the d.c. supply is connected to the record amplifier panel, it also energises a 12V, three-pole change-over relay connected in parallel with it. This relay transfers the connections from the combined replay-record heads from the input to the replay amplifier to the output of the record amplifier. Under normal replay conditions, neither the relay nor the record amplifier panel are energized. The bias/erase oscillator is mounted at the output end of the record amplifier and is supplied with power when this panel is energized. By using separate record and replay amplifiers some additional component cost is incurred, but the internal switching is greatly simplified.

Replay amplifier

The use of the extremely low tape speed of the Philips cassette design, coupled with the small head gaps necessary for good high frequency response, and the

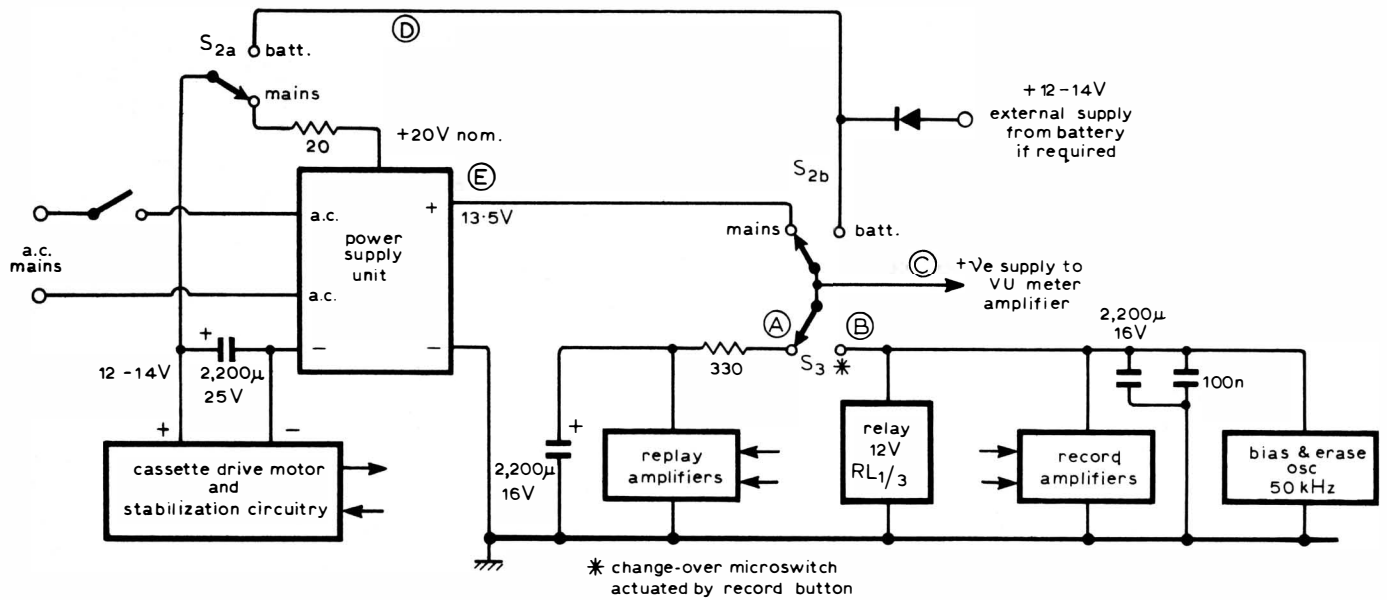


Fig. 1. System diagram showing record/replay switching and battery/mains selection. Motor stabilization circuitry is provided by the makers of the mechanism.

relatively low coil inductance required for adequate recording and bias current, lead to a very low output voltage from the cassette replay heads. In the stereo configuration this means a 0VU (normal maximum record level) output of some 800-1000 μ V, and actual signal levels down to a few tens of microvolts. Under these circumstances, it is imperative that great care is taken, both in the design of the input amplifier circuit and in the layout of the wiring from the heads to this, to prevent obtrusive noise or hum. The use of a d.c. tape motor greatly reduces hum originating in the motor, but the mains transformer in the power supply should have a low external mains field and should be as far away as possible from the replay amplifier input wiring and replay heads.

In the prototype, as the mains transformer which had been obtained was not very well designed from the point of its external 50Hz field, a home-made Mumetal shroud was fashioned from a

surplus c.r.t. screen to enclose it and this completely solved the problem.

The input circuit of the replay amplifier is shown in Fig. 2: the amplifier is optimized for the minimum practicable noise voltage, to which the major contributory factors are Johnson noise, due to thermal agitation in the input circuit and input device base diffusion impedances (minimized by making the input impedance as low as practicable and by the correct choice of input devices – epitaxial-base silicon bipolar transistors are preferred); “Shot” noise, which is proportional to both current and bandwidth; “excess” or “1/f” noise,

due to imperfections in the crystal lattice and proportional to device current and root bandwidth and inversely proportional to root frequency; collector-base leakage current noise, which is influenced both by working temperature and collector-base voltage; and finally surface recombination noise in the base region. Where these are approximately calculable, the equations shown below are appropriate.


Johnson (thermal) noise $V = \sqrt{4KTR\Delta f}$
 Shot noise $i = \sqrt{2qI_{DC}\Delta f}$

Modulation (1/f) noise $V_m = \frac{\sqrt{\Delta I^2 \Delta f}}{f}$

where Δf is the bandwidth (Hz)
 $K = 1.38 \times 10^{-23}$, T the temperature (K), q the electronic charge (1.59×10^{-19} coulombs), f the frequency and R the input impedance.

In practical terms, this means using a silicon bipolar epitaxial-base transistor as the input device, which should be of p-n-p form to take advantage of the

Fig. 2. Relay amplifier.

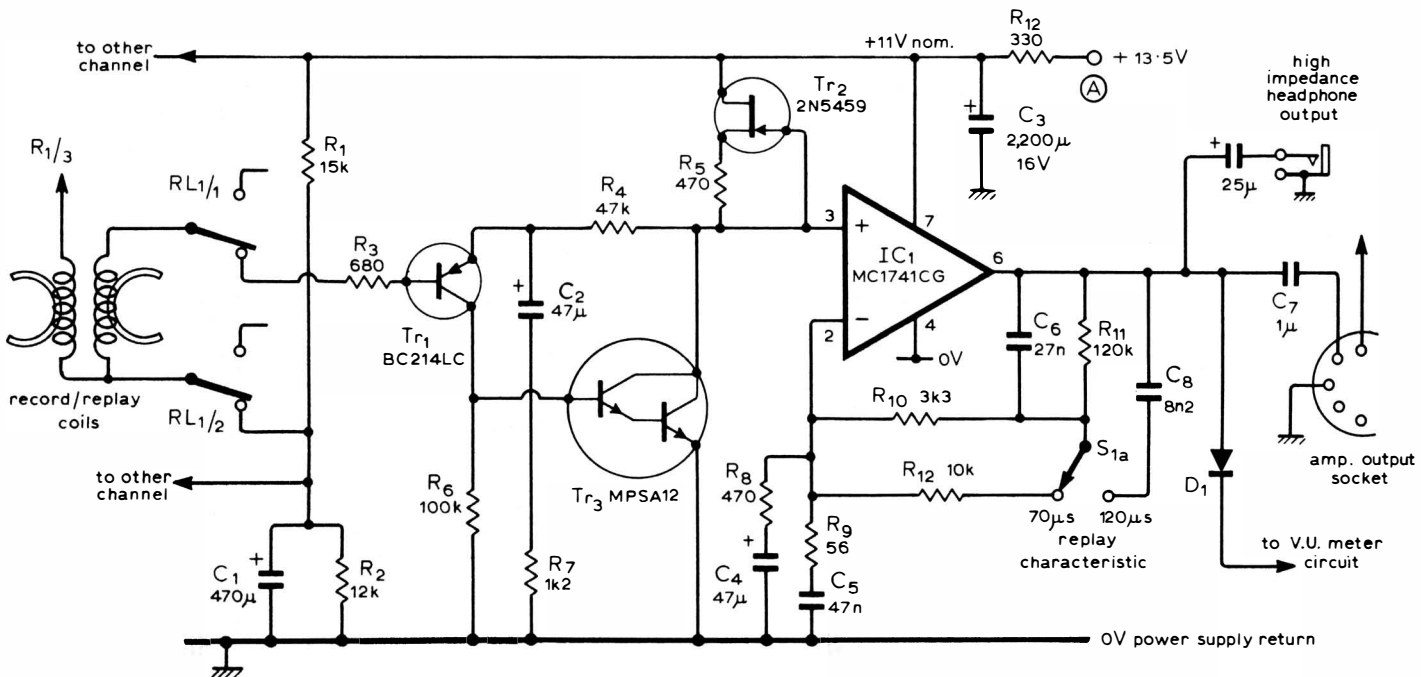

better surface recombination noise characteristics of the n-type base material, at an appropriately low collector-to-emitter voltage, say 3 to 4V, with as low a collector current as is permissible and a base circuit impedance giving a suitable compromise between Johnson noise and device noise figure requirements. In the case of the Texas Instruments BC214LC, the optimum collector current and base circuit impedances are $10\mu\text{A}$ and about 800 ohms. This gave, on the prototypes of this amplifier, a measured noise referred to the input of some $0.2\mu\text{V}$ which is only slightly above the predicted Johnson noise value for the known input impedance and equalized bandwidth. In practice, the input noise introduced by this stage is sufficiently less than that of the tape background for it to be unimportant as a contribution to the overall system noise figure.

In the second stage of this amplifier, where the replay equalization (frequency/amplitude response shaping) is performed, a good-quality integrated operational amplifier "gain block" is employed, as in all the other gain stages of the system. The unit chosen is the Motorola MC1741CG, which is a fairly standard 741 but in an 8-pin TO39 metal-can encapsulation, and is, in the authors experience with these devices, much to be preferred on grounds of reliability. Two equalizing characteristics are provided, having $70\mu\text{s}$ and $120\mu\text{s}$ upper time-constants. Of these, the former is the internationally agreed standard for chrome tape, and the latter is the normal standard for ferric types.

The output from this amplifier, about 0.4volts r.m.s., at 0VU and 660Hz, is taken to the output socket, and the VU meter through an isolating silicon diode. A similar isolating diode on the output of the record amplifier circuit allows the VU meters to be used both on record and replay settings, which is

useful for assessing tape output characteristics, and the recording levels of recorded cassettes.

The two replay characteristics are shown in Fig. 3, and are determined by the switched values of $R_{10, 12}$ and $C_{6, 8}$. Some additional treble lift to compensate for head limitations is given by R_9 , C_5 and gives rise to the part of the curve indicated in Fig. 3.

Although the author has some personal reservations about the use of series feedback configurations in the case of magnetic pick-up input equalization arrangements, where at the upper end of the recorded frequency range it is possible to generate relatively large pickup output voltages with consequent risk of distortion due to common-mode failure, in the case of cassette replay heads the likely output voltages are so small in relation to the input device C_{be} voltage that this is a negligible problem. Also, to design for the lowest practicable noise level, series feedback configurations remain the simplest form to implement, although in higher-speed, higher-output recorder systems it could be worthwhile to introduce feedback, around an inverting amplifier, at a low impedance at the earthy end of the playback coils.

To avoid replay head magnetization problems due to switch-on current surges through the replay coil windings on the charging of an input series capacitor, the replay coil is connected between the input reference voltage source and the base of the input transistor, so that the total current flow through this is limited to the base current of this device – about $0.1\mu\text{A}$. (Head magnetization is less of a problem on record due to the demagnetizing effect of the fairly large bias voltage applied to it during recording. It is, however, important that the time constant of the record output circuit should be shorter than that of the decay of bias voltage, which is ensured by the use of fairly substantial capacitor values on the record amplifier positive supply line.)

The measured total harmonic distortion of the replay amplifier, input to output, at up to 1V r.m.s. output, is less than 0.01%, and a very high degree of

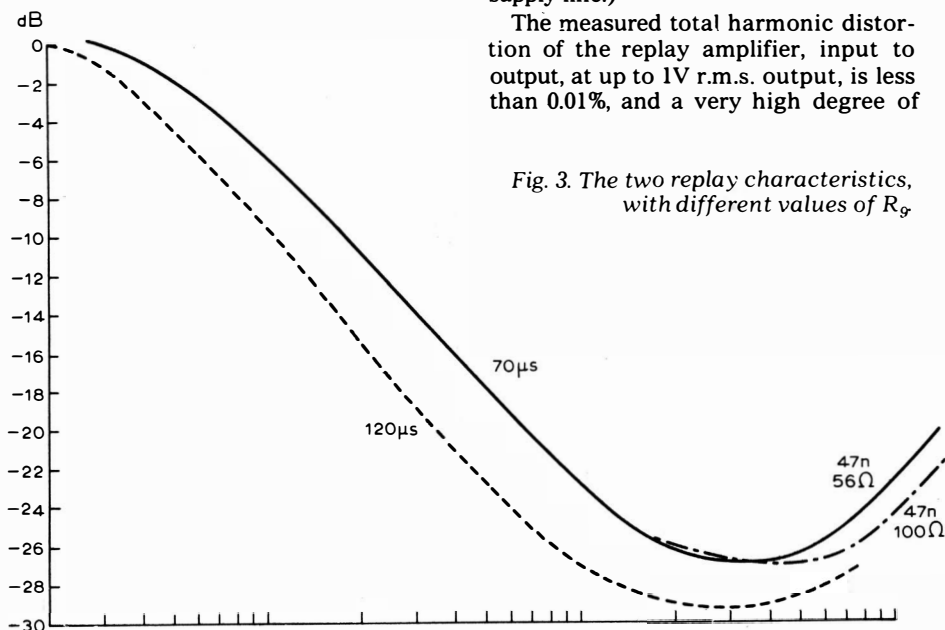


Fig. 3. The two replay characteristics, with different values of R_9 .

Measured performance figures of prototype (Garrard CT4 mechanism)

Frequency response $\pm 1\text{dB}$ 35Hz – 12kHz (BASF LH Super C90)
 Channel separation 45dB at 1kHz
 Erasure better than 50dB
 T.h.d. at 0VU (660Hz) 0.75%
 Replay amplifier background noise, CCIR weighted, –56dB.
 Zero recorded level background noise, CCIR weighted, –52dB.
 Bulk erased tape background level, CCIR weighted, –54dB.
 The above figures refer to a 1kHz tone recorded at 0VU on BASF LH Super C90. Both channels are identical to within 1dB.
 Record amplifier t.h.d. at +3VU less than 0.02%
 Replay amplifier t.h.d. at +3VU 0.01% (Residual distortion less than background noise at –6VU.)

*This figure should be considered in the context of typical disc replay figures (e.g. 1.2% and 0.6% harmonic distortion for 20cm/s at 1kHz, vertical and lateral modulation respectively) for a good-quality pick-up cartridge in a good-quality arm, rather than in comparison with the less than 0.1% t.h.d. typical of a good-quality audio amplifier.

h.t.-line noise and ripple rejection is given by the use of a constant current-source load (Tr_2) in the first stage.

Record amplifier

Since the design value of input sensitivity for this amplifier is not very high – 50mV r.m.s. input at 1kHz for a 0VU record level – great care to obtain a high signal-to-noise ratio is unnecessary (the difference in recorded noise obtained by replacing the input MC1741CG with a very low noise circuit such as that used in the replay amplifier is only of the order of 0.75dB). A simple amplifier design based on a pair of these operational amplifiers is therefore entirely adequate, and confers a number of minor advantages in addition to those of simplicity and economy of component cost.

To avoid the necessity for winding coils for the generation of the required peaky record characteristic (desirable to offset shortcomings in the head performance, tape and recording characteristics at the upper end of the recording range) an active RC circuit arrangement is employed. This is shown in the circuit diagram of Fig. 4, and consists of the network $R_{16}, R_{17}, C_{12}, C_{13}$ in conjunction with R_{19}/VR_2 and C_{15} . The recording characteristics obtainable from this are shown in Fig. 5, for various component values, which may be of use if it is desired to use different record heads to those supplied with the Garrard CT4. The magnitude of the pre-emphasis hump in the 13-15kHz region is determined by the setting of VR_2 (a preset component on the circuit board), while the basic recording treble

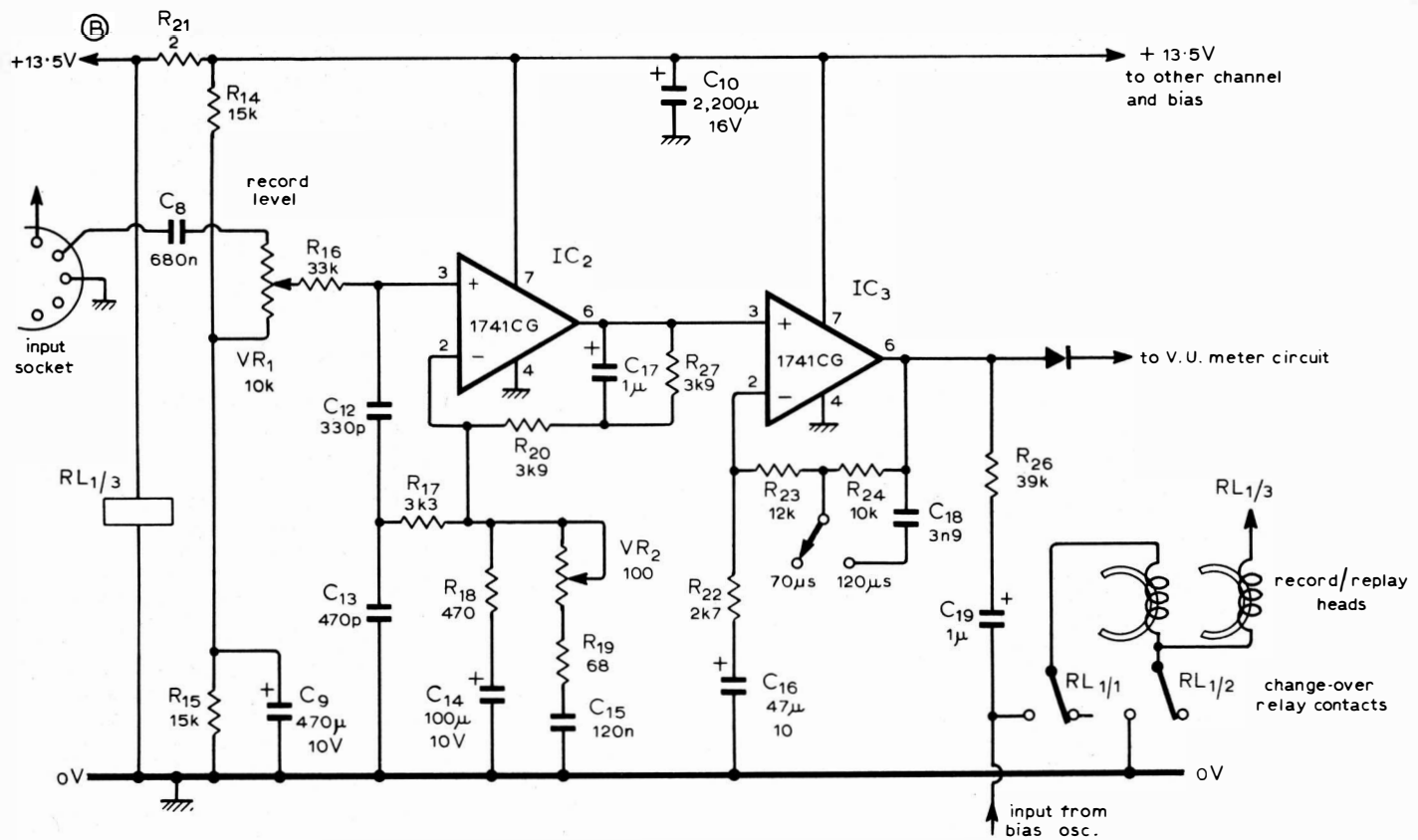


Fig. 4. Recording amplifier.

lift time constants are determined by C_{12} and C_{15} .

Changeover from the basic $70\mu\text{s}$ recording characteristic to the $120\mu\text{s}$ one is by switching C_{18} into circuit. The new cassette-standard bass pre-emphasis at $3180\mu\text{s}$ is provided by C_{17} , R_{27} . A $39\text{k}\Omega$ swamping resistor is interposed between the output of the record amplifier and the head, to approximate to a constant-current recording condition. Since the impedance of the head at the upper end of the frequency range of the recorder is less than $10\text{k}\Omega$, the loss of h.f. due to this is small, and readily compensated for in the equalizing circuitry. With this value of output swamp resistor, attenuation of the bias voltage by the low output impedance of the 1741 is sufficient to eliminate the need for any additional bias-trap circuit, while allowing record amplifier circuit outputs of up to $+3\text{VU}$ with less than 0.02% t.h.d. at 1kHz .

With the recording heads used in the prototype, a 0VU record level at 660Hz , chosen to avoid regions in which pre-emphasis characteristics would influence the result, corresponded to 2.25Vr.m.s. at the output of the recording amplifier. Since the output magnetic flux characteristics of the heads were not specified, this level was chosen arbitrarily as the one at which a third-harmonic distortion level of approximately 1% was given at 660Hz on a good quality (BASF Super LH C90) ferric tape. This gives a $+3\text{VU}$ setting of 3.1V r.m.s. , which is below the amplifier clipping level on 13V supply line voltage.

The output of the record amplifier is taken to the VU meter circuit through a silicon diode, but since the record


output is higher than that of the replay, an attenuator is included in this circuit to bring the two outputs to equality. The $47\text{k}\Omega$ resistor to the zero-volt line serves to provide a forward current to bias the diodes into conduction. Switching between record and replay in the VU meter circuit is automatic since only the circuit in use has an output

above the zero-volt level, the other one being disconnected from the supply line. Unwanted signal transfer through this diode feed network is of a very low order magnitude.

VU meter

This is a straightforward precision millivoltmeter of conventional type, in which the meter rectifier bridge is connected in the feedback loop of an operational amplifier as shown in Fig. 6. Although this is a more elaborate arrangement than most conventional VU meter systems, the cost of the operational amplifiers and the associated germanium diode rectifiers is small in comparison with even a modest twin

Fig. 5. Recording characteristics with variations in C_{15} and C_{12} . The peak heights are adjustable by VR_2 , (b) being the compromise adjustment and (c) the setting for optimum square wave reproduction.

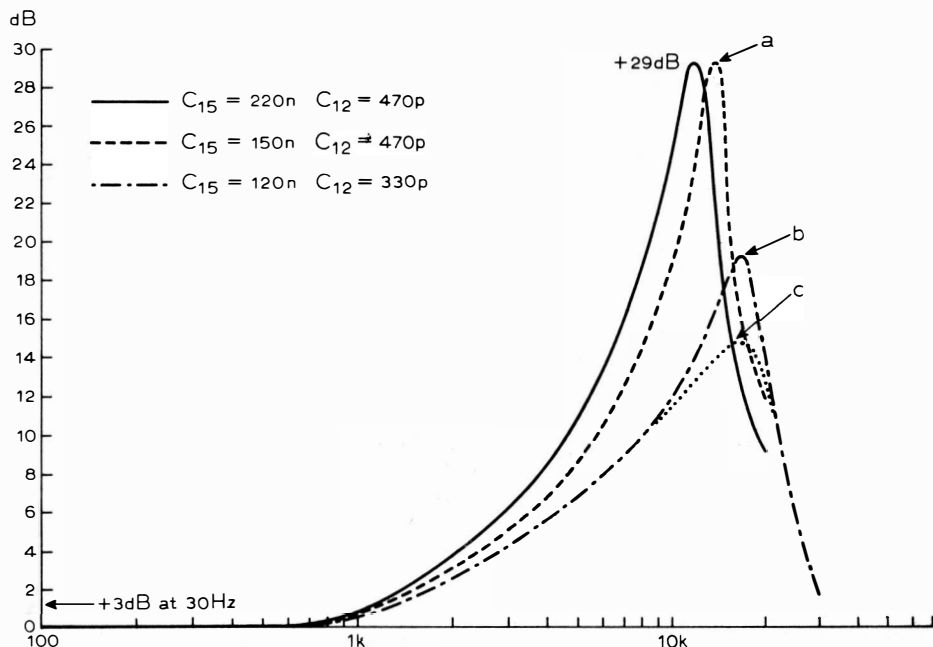

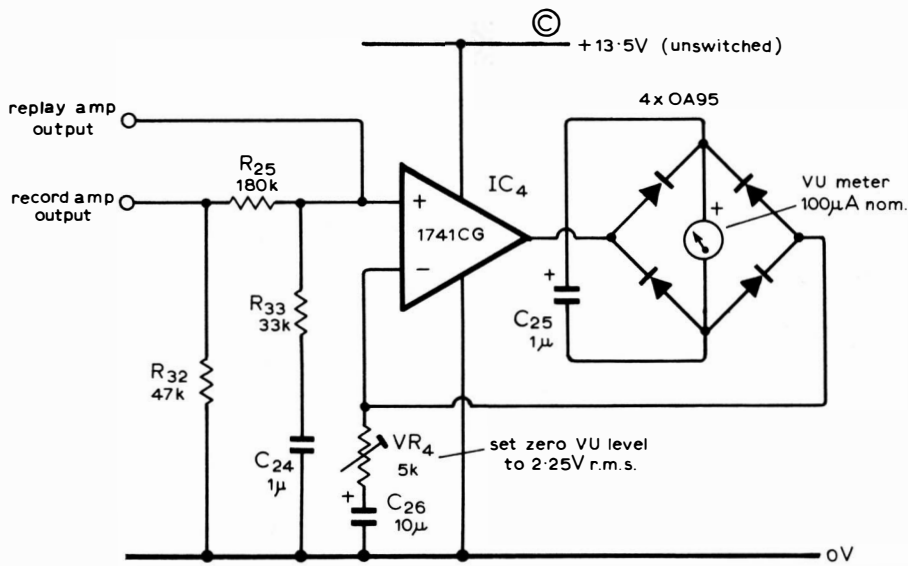


Fig. 6. VU meter circuit.

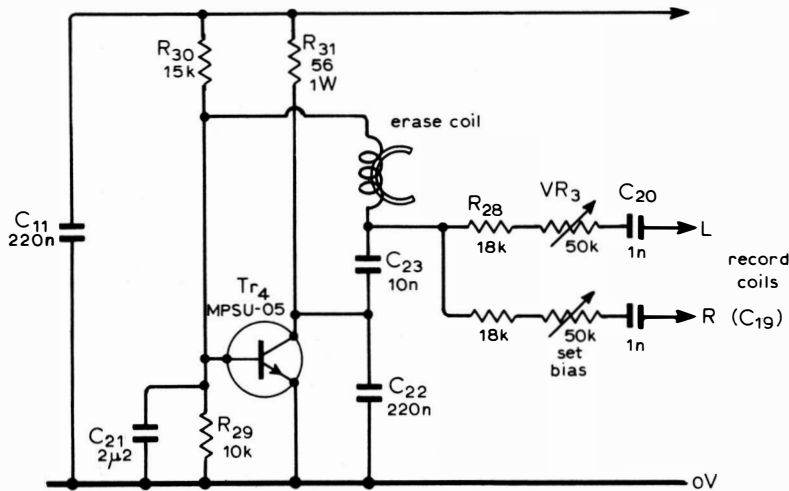


Fig. 7. Erase and bias oscillator, with continuous variation of bias level. Provision is made on the p.c.b. for the level to be switched.

VU meter, and the arrangement has much in its favour in a very linear a.c.-to-d.c. conversion, flat frequency/amplitude response, high input impedance, and short output voltage rise time due to the low output impedance of the amplifier. This latter feature is of particular value in tape recording, where the signal level meter should ideally have zero inertia so that it can follow the modulation of the signal without missing short-duration peak levels.

Bias and erase oscillator

A fairly common and irritating feature of inexpensive cassette recorders is their inability to erase fully an existing programme on a tape, when a further recording is being made on top of this. For satisfactory erasure of ferric and ferrichrome tapes, at least 20V r.m.s. should be supplied to the erase coil, and for chrome tapes a value as high as 25V may be required with typical cassette

erase heads. To obtain voltages as high as this with low-voltage lines, it is customary to use a push-pull oscillator driving a step-up transformer, but some care is necessary to avoid harmonic distortion which can impair the recorded signal quality and s/n ratio.

A simpler method, which avoids many complications, is to use the erase head as the coil in a self-oscillating circuit, and employ the Q-multiplication of the tuned circuit around the erase coil both to provide the necessary voltage swing and also to improve the purity of the waveform. The circuit shown in Fig. 7 is a modified Colpitts, and provides an output of 25-33V r.m.s. at the required erase frequency (50kHz), with supply voltages in the range 12-14 volts and with a waveform distortion of less than 1%, even when loaded with the bias circuitry. The current consumption is, however, of the order of 100mA, giving a transistor dissipation of about 0.7W. The Motorola MPS-U05 is particularly suitable, but other high-

gain, high-transition-frequency 1W devices are quite suitable since the circuit is not particularly critical of component values or types, except in so far that these may modify the operating frequency, which should be within the range 50kHz \pm 5%.

The h.f. bias waveform is also derived from the erase coil, by way of a resistor-capacitor chain, VR₃, R₂₈, C₂₀, to each record head output (VR₃ is twin-gang). Since the purity of the bias waveform at the recording head is the design requirement, it is tempting to use a value of series capacitor (C₂₀) which will be series resonant with the record coil at the bias frequency, as is fairly standard commercial practice. However, on reflection, confirmed by measurement, it is better to use a larger value of C₂₀, and take advantage of the integrating characteristics of the series network to attenuate higher order distortion components in the bias waveform, as seen at the head.

The bias voltage required across the record coil is dependent on the tape used but, as a guide, should be in the region 5-7V r.m.s., with the CT4 heads. The signal level, for reference, at this point, is only about 50mV.

(To be continued)

Garrard Engineering Ltd now tell us that production of the CT4 mechanism is to stop in June. As mentioned in the article, however, Goldring Ltd also market a unit made under the Staar patents and this will continue to be available for some years. The type number is CRV and one difference between the two is that the CRV does not incorporate motor speed stabilization. An easy way to overcome this is to use the SGS-Ates TCA910 regulator i.c. on a small p.c.b., the design of which we will publish in the next article.

Wireless World has arranged a supply of stereo glass fibre p.c.bs for this design. The boards measure about 9in x 3¼in and accommodate the changeover relay as well as two pre-set potentiometers per channel for switchable bias settings. One-off price is £4.50 inclusive from M. R. Sagin, 11 Villiers Road, London NW2.

Automation in broadcasting

In addition to the International Broadcasting Convention being held in London, September 20-24, there is to be an international conference on automation in sound and video broadcasting and transmission networks held in Paris, October 19-21. Papers are still being invited and anyone wishing to contribute is asked to contact Mr B. Sewter, IBA Engineering Headquarters, Crawley Court, Winchester, Hampshire (Tel: Winchester 822477).

Low-noise, low-cost cassette deck — 2

by J. L. Linsley Hood

Any convenient power supply circuit may be used for a.c. mains operation, provided that it can be set to give a stable, ripple-free output of 13.5-14V at output currents up to 250mA. A suitable design is shown in Fig. 8. The low-value resistor in the record amplifier supply line is to limit the supply line current surge through the changeover micro-switch when the large capacitor on this line is connected in parallel with the capacitor on the output of the power supply. To avoid noise originating from the pulsating current demand from the d.c. cassette-drive motor-control circuitry, the recorder supply is taken directly from the power supply reservoir capacitor through a 20Ω, 10W resistor, with the negative return line being also directly connected to the reservoir capacitor, rather than to a chassis return.

The chassis itself is only connected to the zero-volt line at the input to the replay amplifier.

Recording and bias levels

One of the most obscure areas in the field of tape recording, in the eyes of the layman, is the interaction between tape types and biasing levels. While much


information has been published on this subject, it is often discussed in obscure terms which make the argument difficult to comprehend. Since it is possible that the construction of a cassette recorder of this type may be of interest to those with no previous experience in this medium, an attempt has been made to provide a simple introduction to this topic.

In general, it is not practicable to obtain an adequate remanent magnetic flux in a magnetic tape, for the reproduction of signal waveforms of low harmonic distortion and good output level, unless a high frequency "bias" of suitable magnitude is superimposed on the signal at the time of recording. The effect upon the various signal parameters of variations in the bias level is shown in schematic form in Fig. 9. From this it will be seen that there is not a single biasing level which is optimum for all recorded frequencies, and that the optimum level for 1kHz is in excess

of that which gives the highest output for, say, 10kHz. Also, the level which gives the lowest recorded noise level is less than that which gives the lowest t.h.d.

It is apparent from this that the setting of this parameter is one which demands some compromise, and the one which is chosen will depend upon the preferences of the user. In general, for cassette recorders, the chosen bias is that which gives the maximum output at 330Hz, or a slight excess of that optimum for 1kHz, and the reduction in output at higher frequencies is compensated by modifications to the record pre-emphasis curve. However, the required bias and compensation characteristics will be different from one make of tape to another, and from one design of record/replay head to another. In this design, the decision had been taken, partly in the interests of running costs, and partly in the interests of minimizing wear in the Permalloy heads, to optimize the design for "ferric" tapes rather than chrome types, and the Philips standard low noise C90 was taken as the reference. It was found, however, that the settings derived for this was also optimum for

Fig. 8. Power supply. The motor is fed with 3.5V by the stabilizer, but the solenoid is provided with the full 12-14V.

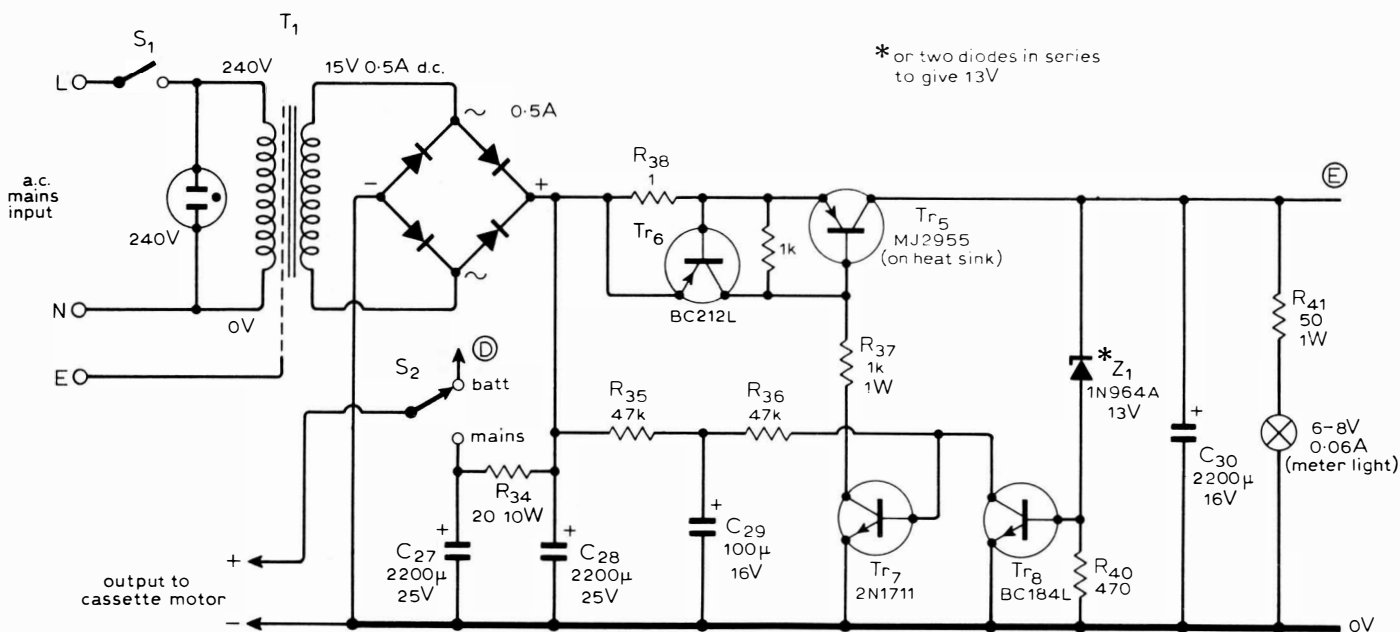

“super” tapes of the types exemplified by Memorex MRX₂, and BASF Super LH, although these gave an improved performance.

In general, there is very little difference in the background “bulk-erased” noise levels of most good-quality commercial cassette tapes, although there will be larger differences between the noise outputs of tapes passed through a recorder set to record at zero signal level. The greater the degree of homogeneity of the tape oxide layer, the lower the zero-recorded-level noise will be, down to a minimum which depends on the fundamental granularity of the oxide medium. The recently introduced “super” series tapes have a more uniform oxide coating, which can give a 1-2dB zero-signal background level improvement.

However, there are also improvements which have been made in the output level and harmonic distortion for a given output level, due to a more careful balance of grain shapes and sizes. The extra 2-3dB in output can lead, in total, to a small though audible improvement in overall signal-to-noise ratio (some typical results are shown in Fig. 11, and Table 1.) Useful though this is, a far greater capacity for improvement in overall performance lies in the hands of the user in a careful choice of the recording level setting. Ideally, one should record at as high a level as possible, so long as few signal peaks significantly exceed the DVU level. A 1-2dB excess is unlikely to be noticed in replay, especially with good tape, provided that the duration of overrun is brief, and the difference in s/n ratio from “correct” to over-cautious choice of record levels can readily exceed the difference between a cheap tape and an expensive one.

Probably the best way of choosing recording levels is to set the mechanism to Record but with the pause button pushed in, and in this condition to experiment with the gain settings until the optimum setting is found. when the recording can be started. In the case of a live performance, assuming one has the co-operation of the performers, it is usually possible to persuade them to execute a known fortissimo and set the record levels appropriately for this.

Noise characteristics of the system

During the development of this circuit, the sources of noise in the system were investigated at some length, since, although it was envisaged that some form of external noise-reduction system would be incorporated for use during replay, it seemed advisable to try to minimize noise in the design before taking additional palliative action. The reduction of noise in the replay circuit has already been described; if the unweighted noise level at this stage, without tape, is taken as the unit, the bulk-erased-tape noise level corresponds to about one and a half or two units, and the zero-record-level noise

(with the circuit parameters arranged in accordance with normal practice) was then equivalent to some five or six units.

Obviously there was little that could be done about the noise level of the tape, as received, but it seemed that quite a lot could or should be done about the 14dB worsening of this during no-signal recording. Indeed, if it were possible to get down to the level of the original tape, the overall performance would have been beyond reproach, in

spite of the low tape speed and narrow tape width. An additional piece of evidence which seemed of interest was that the replayed noise was “whiter” than would have been expected from an original white-noise source (i.e., the tape) when replayed through the type of equalizing characteristic employed in the replay amplifier. This seemed to be a common characteristic of commercial cassette recorders, which all sounded “whiter” on the replay noise tone than

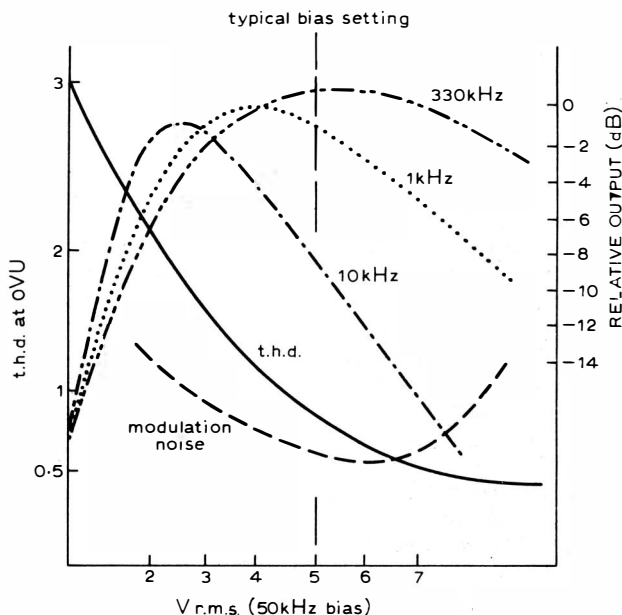


Fig. 9. The effects of changes in the h.f. bias level on output, t.h.d. and modulation noise.

Fig. 10. Record/replay frequency/amplitude curves for a variety of tapes, optimized for maximum flatness and for best square-wave reproduction

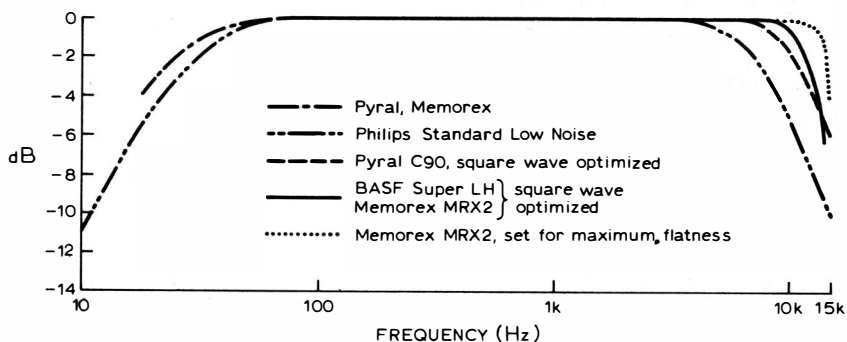


Table 1.

Relative output at 660Hz (0VU recording level)	
Philips Standard C90	0VU (+0dB)
Pyral C90	+ 2dB
Memorex MRX ₂ C90	+ 2dB
BASF Super LH C90	+ 3.5dB

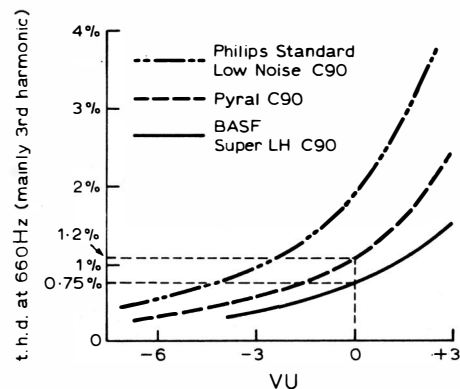


Fig. 11. Harmonic distortion (including noise) as a function of recording level for three types of tape.

0VU = 2.25V r.m.s. @ 660Hz at output of record amp

seemed reasonable to expect. It was also observed that changes in the level, frequency or shape of the bias waveform made no difference to the result. The conclusion began to grow that the problem was due to generally-distributed noise, in the source and record amplifier, being selectively amplified in the 10-15 kHz band and applied to the tape at high levels through excessive signal pre-emphasis.

Having become convinced on this point, the attempt was made to determine the optimum compromise between flatness of frequency response and signal-to-noise ratio for a given record level. At this stage it was found that optimization of a recorded 1kHz square wave to reduce the initial overshoot and ringing found when more conventional magnitudes of pre-

emphasis were applied gave also the best performance compromise on bandwidth against s/n ratio. The bias levels found during this exercise were compared to those obtained by more conventional setting-up procedures, and found to be substantially identical. However, the zero-signal-level recorded noise was found to have been reduced by about 10dB by the process of square-wave optimizing, as compared to that given by frequency response optimizing. The two curves are shown in Fig. 10, and it will be seen that the h.f. loss amounts to only 1dB at 10kHz and some 4dB at 14kHz, which can be remedied by the use of amplifier tone controls on replay with very little detriment to performance.

The final conclusion is that in general far more h.f. pre-emphasis is employed

on recording, in the interests of maximum flatness of the published response curves, than is sensible in the light of the overall performance, and that with more prudence exercised in this respect, noticeable improvements could well be made. Interestingly, programme recordings made before and after optimizing of the square-wave performance of the recorder did not show the expected small loss of higher frequencies, with the upper register seeming both cleaner and more extended than before, possibly due to the lessening of the incidence of h.f. tape or head saturation.

One final recommendation in this respect is that for one's own use, even on ferric tapes, the 70 μ s characteristic should be used both on record and replay. However, this is a choice which can be assessed readily by individual experiment. Certainly, in the case of the author's prototype, the use of this equalizing time-constant, in association with an optimized square-wave characteristic, has given a system in which the tape noise, on a good quality tape, is sufficiently unobtrusive to render further noise reducing circuitry unnecessary.

Bias and equalization settings

It will be apparent from Fig. 9 that adjustment of the h.f. bias level of the recorder will have the effect of altering the whole response curve, by altering the effective recorded levels of the h.f. and l.f. components relative to one another, and it may therefore appear difficult to optimize either the bias or the equalization. The suggested method is therefore as follows:

- Set VR₂ so that the response curve on record is as curve A on Fig. 5., (approx. 85 Ω) when measured at the output of IC₃.
- Set the bias level so that there is approximately a 1-2dB drop in output at 1kHz.
- Record a square wave at 660Hz, and make small adjustments to VR₂ until the cleanest leading edge is obtained on the replayed square wave, with only a small single overshoot.
- Finally, leaving VR₂ set at the chosen value, record a 660Hz square-wave at various bias levels and adopt the one which gives the best overall square-wave shape for the tape which it is desired to employ.

The technique of square-wave optimization is well known in the audio field as a means for setting tone-controls and filters to optimum flatness, because of the facility which it offers for a simultaneous examination of a wide range of frequencies. On exactly the same score it would appear to be an excellent method of optimizing bias levels.

While it is hoped that the performance given by the prototype will prove to be fairly typical of the results given by other models built to this design, it is appreciated that in a system in which


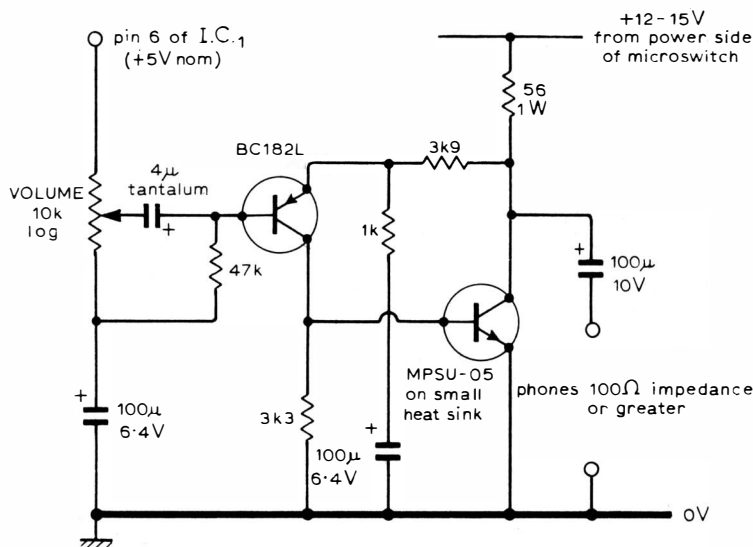


Fig. 12. Class A headphone amplifier, with a gain of 5.

Fig. 13. Low-noise microphone pre-amplifier.

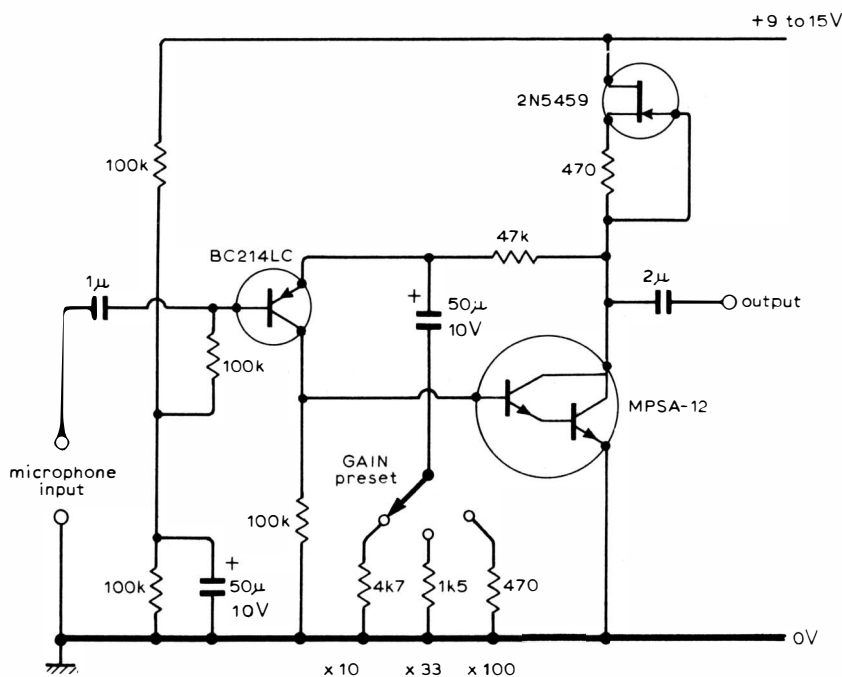

not only will components vary in types and tolerances, but also the tape transport mechanism and heads (which may be changed during the manufacturer's production run for reasons of commercial availability) may differ from those used by the author, the scope for variability is considerable. Also, from personal experience, and measurements, there is a considerable variation in performance from one tape type to another, although the consistency of performance of the better-grade tapes from the better manufacturers appears to be fairly good. On the credit side may be set the fact that one does not have quality control problems in a unit that is one-off, and that one can optimize one's channel balance and h.f. performance for the tapes one prefers and the heads one happens to possess.

Headphone operation

Both the output level and the drive capability of the final 741s of the replay amplifier are adequate to give a satisfactory signal strength and quality into the 2kΩ load impedance of the author's headphones (Sennheiser HD414), so, for simplicity, this was the course adopted. However, for those with lower-impedance or less-sensitive headphones, a suitable circuit is shown in Fig. 12. This operates in class A, and is suitable for load impedances down to 100 ohms.

Direct microphone recording

The sensitivity of the record input is only intended to be sufficient for recording from an existing audio amplifier or radio tuner capable of delivering some 50-100mV output at a fairly low impedance, and it would not be suitable for microphone inputs. For this purpose a pre-amplifier can be used, of which a suitable circuit is shown in Fig. 13. Three preset gain positions are given, of 10, 33 and 100×, which should cope with the bulk of microphones likely to be found in practice. A typical gain suitable for a low-output cardioid capacitor electret microphone is of the order of 33, for a normal recording level at half-gain setting on the recorder.

Final details of the design will be in the final part, including information on the motor controller – lack of space prevents publication in this issue.

We are informed that components and metalwork for this design will be available from Hart Electronics, Penylan Mill, Oswestry.

Appendix

Derivation of record equalisation characteristics.

The generation of a recording pre-emphasis characteristic of the general form shown in Fig. 5 is normally done by incorporating a damped LC parallel resonant circuit in the feedback loop of an inverting amplifier stage. However,

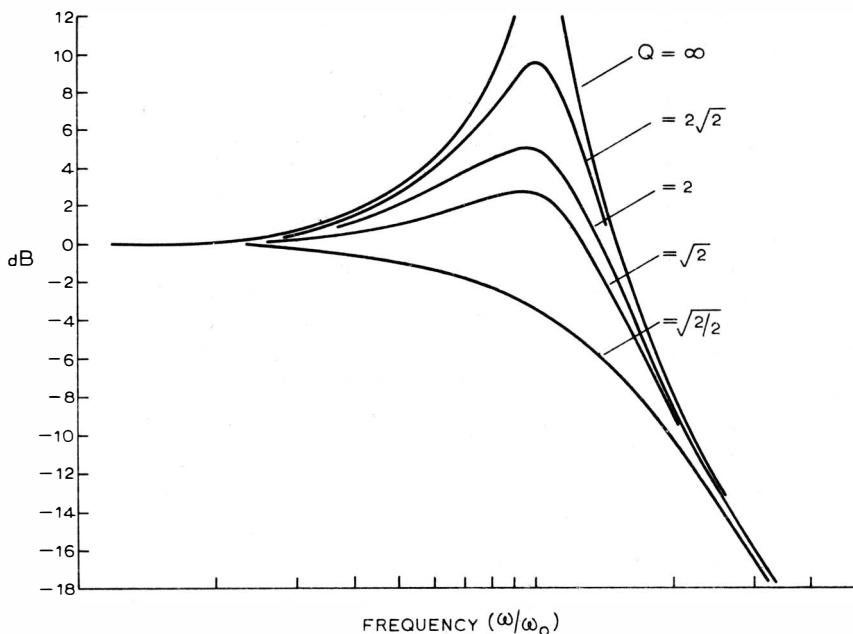


Fig. 15. Frequency/gain response of filter in Fig. 14.

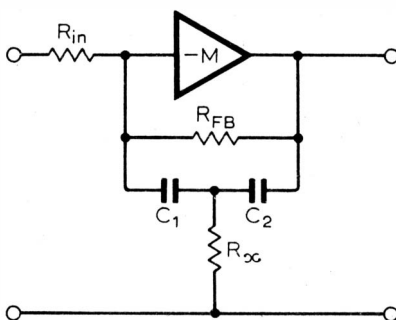


Fig. 14. Basic second-order active low-pass filter (as Reference 1).

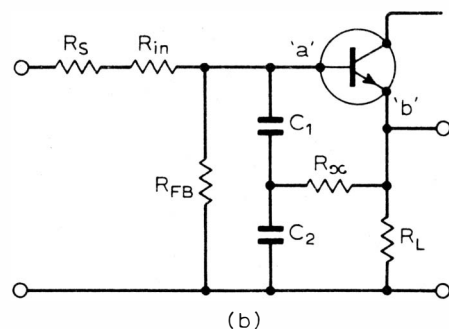
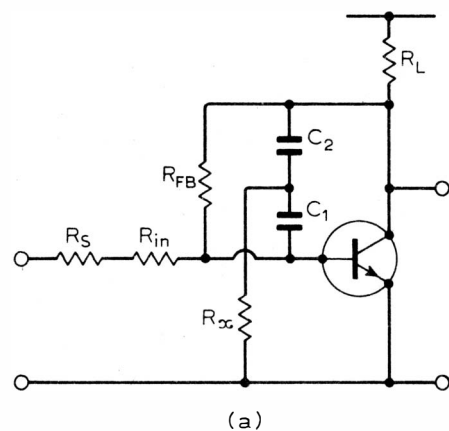


Fig. 16. Common-emitter (a) and common-collector (b) arrangements of basic circuit shown in Fig. 14.

since it was desired, in the interests of simplicity, to avoid the use of inductors, and it was also required to avoid possible trouble due to the intrusion of 38kHz signals from multiplex stereo decoders, the decision was made to use the gain/frequency characteristics of an under-damped second-order active low-pass filter, such as that shown in Fig. 14.

This is one of the classic forms of active element, and was analysed by Girling and Good¹ in the first part of their survey of active filters in *Wireless World*. It has a gain/frequency response of the type shown in equation (1) and

illustrated in Fig. 15 for various values of Q (1/α)

$$\frac{V_{out}}{V_{in}} = \frac{1 + j\alpha \frac{\omega}{\omega_c}}{1 + j\alpha \frac{\omega}{\omega_c} - \left(\frac{\omega}{\omega_c}\right)^2} \quad (1)$$

If this is redrawn, ignoring biasing, in the form in which the amplifying element is a single, common-emitter-connected transistor, as shown in Fig. 16(a), it will clearly be seen that this can be rearranged into the common-collector form of Fig. 16(b) without significant alteration of the expression for the

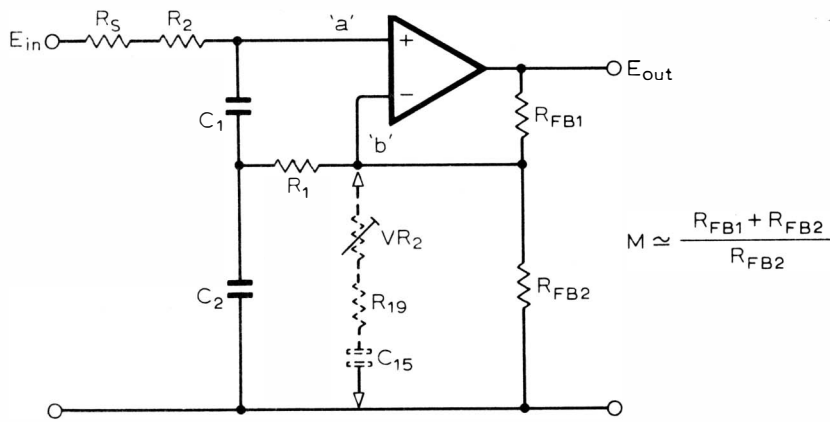


Fig. 17. Use of the active filter in a stage possessing gain, as in Fig. 4.

frequency response. (It was pointed out by Girling and Good that a similar rearrangement leads to the evolution of the filter circuit due to Sallen and Key² from the type based on a feedback loop containing an integrator and a lag, described earlier by Baxandall³.)

Filters of the type shown in Fig. 14, and 16(b) were used in the authors "Modular preamplifier" design (*Wireless World* July 1969) and the subsequent postscript to this and the earlier class A amplifier, published in December 1970. The performance of the circuit shown in Fig. 16(b) referred to as a bootstrap or "H" filter, was analysed by the author in another place⁴ and, in a

different context, by Hemingway⁵.

The operation of the filter circuit of Fig. 16(b), like that of the Sallen and Key configuration, can be realised by any active element in which there is approximately unity gain between points "a" and "b". This allows the use, for example, of a voltage-follower operational amplifier as the active circuit element, or even a non-inverting operational amplifier having more than unity gain, as shown in Fig. 17, provided that an adequate feedback gain margin is available at the frequency of interest. The gain and frequency of maximum response of such a circuit is given by equations (3) and (4) where M is the

normal gain of the stage with feedback.

$$f_c \approx \frac{1}{2\pi \sqrt{[C_3 C_4 R_1 (R_2 + R_3)]}} \quad (3)$$

$$\left| \frac{E_{out}}{E_{in}} \right| = M \left(1 + \frac{(R_2 + R_3)}{R_1} \frac{C_1 C_2}{(C_1 + C_2)} \right) \quad (4)$$

While, basically, the Q of the system is determined by the ratios of $R_1 : R_2 + R_3$, in a stage with a shunt network, such as that of VR₂, R₁₉ and C₁₅ in Fig. 4, the gain will change in the frequency region of the filter attenuation band. The associated phase shift due to this network also modifies the Q and allows adjustment of this by VR₂, which is a feature of some practical convenience.

References

1. Girling, F. E. J., and Good, E. F., *Wireless World*, vol. 75, No. 1406, pp 348-352.
2. Sallen, R. P., and Key, E. L., *Trans. IRE.*, vol. 2, No. 1., pp. 74-85.
3. Baxandall, P. J., *Wireless World*, vol. 61., No. 1., pp. 8-14.
4. Linsley Hood, J. L., *Hi-Fi News and Record Review*, vol. 18, No. 2., pp. 293-294.
5. Hemingway, T. K., *Electronic Designers Handbook*, pp. 283-288.

Component supplies

Goldring-Lenco CRV cassette mechanisms can be obtained from Goldring Ltd, 10 Bayford St, Hackney, London E83SE, or Hart Electronics, Penylan Mill, Oswestry, Salop. VU meters are available from J. E. T. Electronics, 90a Mawney Road, Romford, Essex.

Books Received

According to its sleeve note **Problems and Solutions in Logic Design** by Prof. D. Zissos, makes easy and reliable logic design techniques available to those with no specialist knowledge of mathematics or engineering. Even those who are not familiar with Boolean algebra will find an appendix giving sufficient foundation for the rest of the book. The emphasis throughout is on optimal rather than strictly minimal designs which have become less important with the availability of integrated circuits. In the case of sequential circuits, these allow hazard-free designs for the realistic engineering constraint of a maximum variation of 33½% in gate speed. A feature of the book is the comprehensive set of problems and solutions at the end of each chapter. These have been chosen to appeal to the student and include the design of logic circuits for traffic lights, a panel game, digital clocks and electronic dice. For the practising engineer solutions are given for commonly used circuits such as flat sorters, shaft encoders and counters. After an introduction to the basic concepts of logic design, the chapters deal with unclocked sequential circuits, clocked sequential circuits, counters and combinational circuits. The design pattern used

throughout the book was developed by Prof. Zissos several years ago and is now gaining rapid acceptance. The technique involves the conversion of a design problem into a flow diagram which can be converted directly into the basic logic equations before the circuit is then drawn. The three stages are analogous to flow charting, writing the software statements and executing a computer programme. An important feature is that the documentation is inherent in the design. The use of state diagrams and sequential equations eliminates confusion in verbal statements. Price £1.75. Pp.146. Oxford University Press, 37 Dover Street, London W1X 4AH.

High Speed Pulse Techniques by J. A. Coebin describes the nature of pulse signals and the deliberate or inadvertent processing of them. The emphasis is on an appreciation of circuit and system behaviour at very high and ultra high speed. It is assumed that the reader is familiar with a.c. theory, use of the Laplace transform, small-signal transistor response, and the fundamentals of logic. Price £5.00 (£3.50 paperback). Pp. 219. Pergamon Press Ltd, Headington Hill Hall, Oxford, OX3 OBW.

Noise and Fluctuation in Electronic Devices and Circuits by F. Robinson. Noise to the physicist represents a phenomena described by statistical mechanics. To the engineer, noise is an obstacle in the realization of useful devices. This book attempts to interest

the physicist and be sufficiently practical for the engineer. The emphasis is entirely on the physical origins of noise in electronic devices, and the way noise behaves in electronic circuits which are used as building blocks. Price £8.50. Pp. 246. Oxford Books, 37 Dover Street, London W1X 4AH.

Japanese Consumer Electronics — Schematic/Service Manual. This publication contains details and schematic diagrams for about 90 products manufactured by J.V.C., Lloyds, Midland, Panasonic, Sanyo, Sharp, Sony and Toshiba. Items covered are digital clock radios, a.m.-f.m. radios, monochrome television receivers, cassette recorders, eight-track tape players and receivers. Four chapters deal with radio principles, radio, recorder, and stereo servicing, transistor and i.c. cross references, and typical circuit diagrams. Foulsham-Tab Ltd, Yeovil Road, Slough, Bucks SL1 4JH.

Recent additions to the **Tab Books** range are **Radio Astronomy for the Amateur** by Dave Heiserman (No. 714, \$5.95 paperback). **Transistor Theory for Technicians and Engineers** by A. Veronis (No. 717, \$5.95 paperback). **Computer Programming Handbook** by P. A. Stark (No. 752, \$8.95 paperback). **Handbook of Multichannel Recording** by A. Everest (No. 781, \$7.95 paperback). **Toshiba Colour TV Service Manual Vol. one** (from 1970 to 1974, \$5.95). Tab Books, Blue Ridge Summit, Pa. 17214, U.S.A.

Low-noise, low-cost cassette deck — 3

Motor control and further notes

by J. L. Linsley Hood

In response to one or two queries, the following notes are offered. Several cassette decks have now been completed, using alternative designs of printed board, and have proved very successful.

Motor control

Circuitry for the control of the drive motor and solenoid is shown in Fig. 20. It is required to supply or withhold current from the cassette-retaining solenoid and to supply a constant drive to the motor in the presence of supply variations.

Solenoid control. Tr₃ normally conducts and energizes the solenoid. As the motor turns, the pulse-generating switch in the mechanism (yellow and green leads in the Goldring deck) keeps Tr₁ conducting, which cuts off Tr₂ and allows current to flow through the solenoid and Tr₃. When the motor stops, so does the switch: Tr₁ ceases to conduct and, after 3 seconds (C₂R₅) Tr₂ conducts, cutting off Tr₃ and de-energizing the solenoid. The cassette is

thereby released. If the "pause" contacts are made, the motor stops, but the cassette is retained in position.

Speed control. The motor is supplied with constant current via Tr₅. Tr₄ is conducting. Back e.m.f. developed by the motor beginning to turn is applied to Tr₄ emitter, reducing its forward bias.

This reduces the current into Tr₅ base and tends to reduce the motor speed — the effect is to stabilize the motor. Tr₅ behaves as a constant-current source by virtue of the feedback from its collector to Tr₄ base.

Record input impedance

There are, unfortunately, two conventions on the impedance levels employed for signal handling prior to tape recording. Of these, the older, and I think the

Fig. 19. Buffer amplifier to match a DIN source to the recording amplifier.



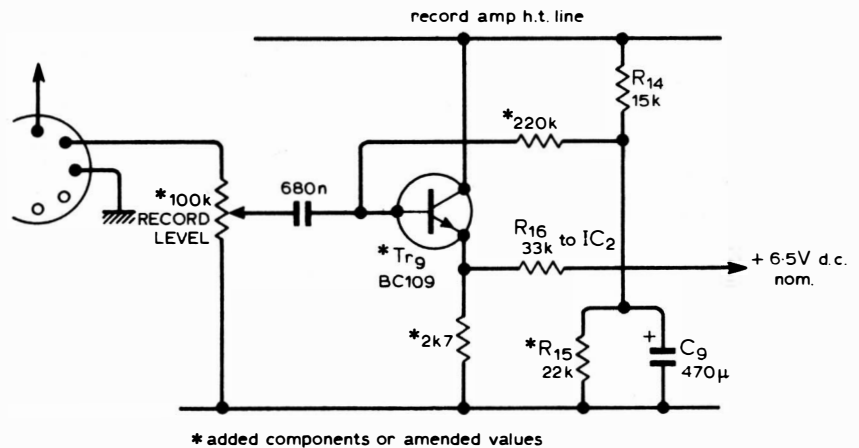
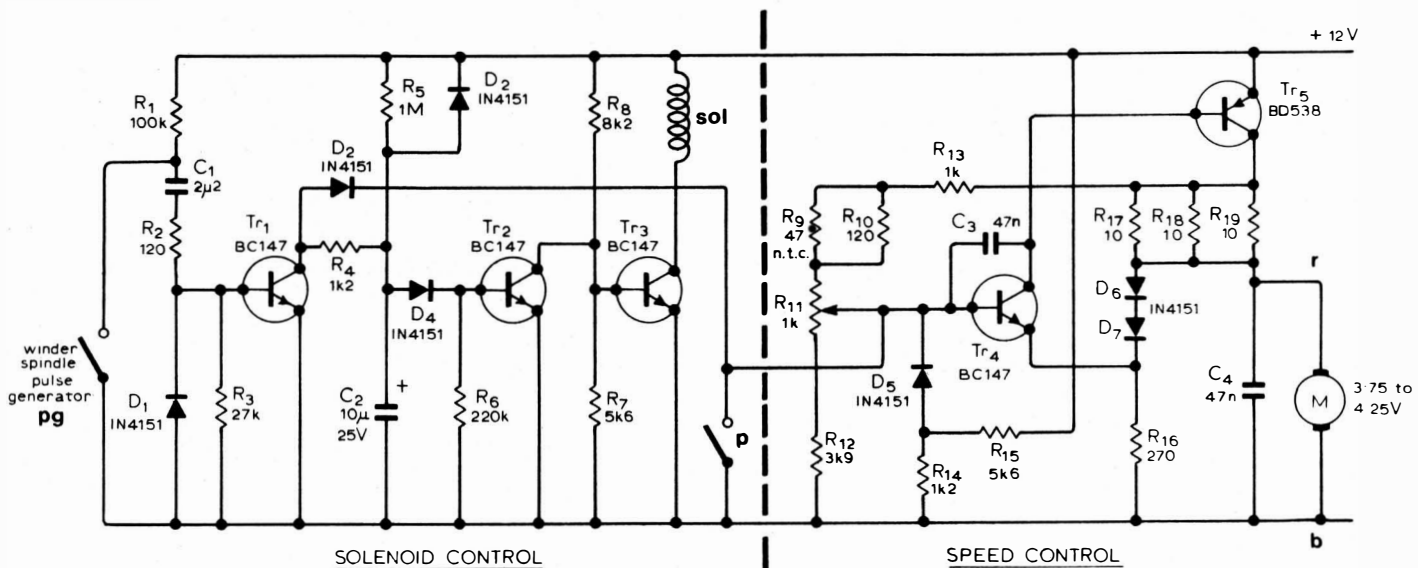


Fig. 20. Circuit diagram of the motor controller.

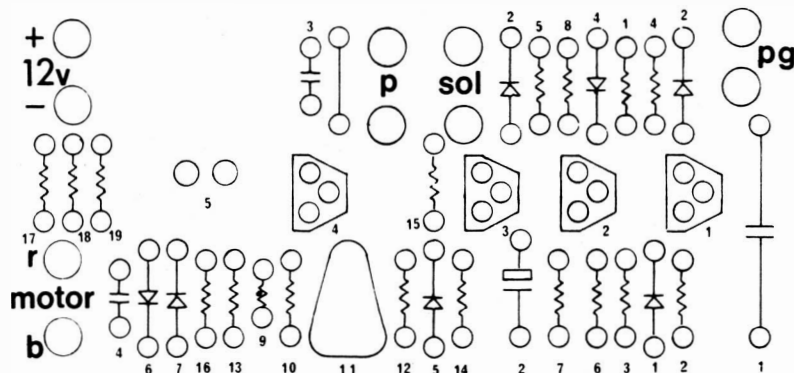

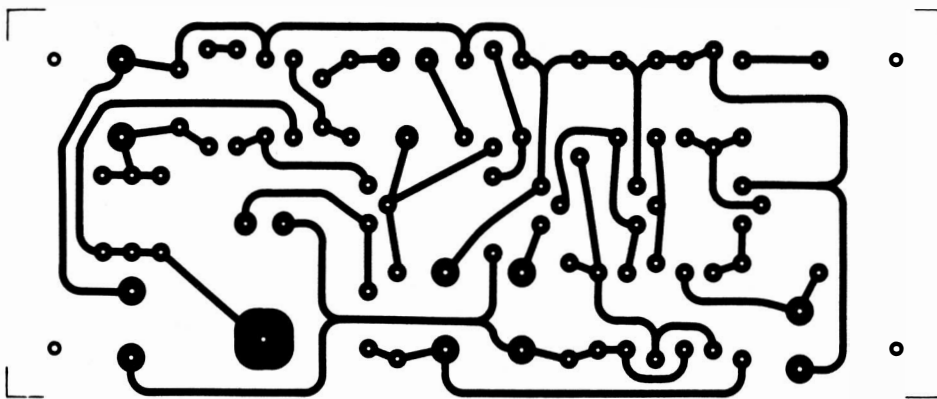

more sensible, is the "600 ohms, 0 VU" (+0 to -60dB, ref. 0.77 V r.m.s.), system which seems to be used by many recording studios, and gives a signal level which can be handled comfortably without problems of degradation due to noise. The other, and the one which is being used increasingly in commercial amplifier "recorder" outputs, is the DIN standard, which implies basically a constant-current source, developing a nominal 1mV r.m.s. for each 1k Ω of recorder input impedance. Predictably, this leads to a degradation of signal quality due to thermal noise unless fairly high value input impedance circuits are employed.

The convention for which the recorder described above was designed was the 600-ohm source impedance one although, taken in general terms, this means any range of source impedances in the range zero to a few kilohms, and the system as it stands would probably have inadequate gain if operated from a DIN source. It is, however, not practicable simply to increase the input record level potentiometer to 50k Ω or 100k Ω since the source impedance of IC₂ influences the Q of the h.f. pre-emphasis system (see Appendix). While the effect of the existing 10k Ω potentiometer, when driven from a fairly low source impedance, is negligible, this would not be true for a higher value DIN input.

If, therefore, this is to be used with a commercial unit having this convention (as distinct from a home-constructed item, in which it is probably most convenient to take the recorder feed at the pre-amp output, in parallel with the power amplifier input), it is recommended that a small buffer circuit

Fig. 21. A suggested, actual-size layout for the controller. The layout and modifications to the speed control circuit are due to Mr A. H. Milligan.

should be attached to the output of the record level potentiometer, as shown in Fig. 19.

Replay h.f. stability

Proximity of output and input leads may cause instability in the replay amplifier. If this cannot be avoided due to layout constraints, a small capacitor (330pF or so) can be connected across the replay output relay terminals (RL₁/1, RL₁/2) - across the replay coil output in the replay position - without any adverse effect on the h.f. performance.

The author has pointed out to us that the use of a Doram 207-374 toroidal transformer greatly eases the problems of hum elimination. Doram Electronics Ltd, P.O. Box TR8, Leeds, are the suppliers. Components and metalwork for this design will be available from Hart Electronics Ltd, Penylan Mill, Oswestry, and Powertran Electronics, Portway Industrial Estate, Andover, Hants, also tell us they intend to produce a kit of components. *Wireless World* has arranged a supply of glass fibre p.c.bs based on the author's design. The board accommodates a changeover relay and four preset potentiometers for switchable bias and provision has been made for a single time constant suitable for chromium dioxide tape (70 μ s). The board is priced at £4.50 inclusive. Make cheques or postal orders payable to M. R. Sagin at 11 Villiers Road, London, N.W.2.

Announcements

Customs and Excise have issued a revised list of electronic components which will attract a VAT rate of 12½ per cent from July 1. The announcement supersedes one made on May 22 by the customs and the Electronic Components Board, and the list includes c.r.t.s, radio and tv tuners, delay lines, transformers, chokes and coils, valves and voltage multipliers. The full list is available from the nearest VAT office.

Computer exhibition COMPEC has been acquired by the publishers of *Wireless World*, IPC Business Press Ltd, from the original promoters Trident Conferences & Exhibitions Ltd. This year it will be held at the new Wembley Conference Centre, November 23 to 25. In May COMPEC Europe was launched in Brussels and plans are in hand for further European shows.

The European Physical Society has awarded the Hewlett Packard Europhysics prize to Professor Wolfgang Helfrich for work on liquid crystals, leading to the discovery of the twisted nematic display.

The Sira Institute, in association with Warren Spring Laboratory, is holding a two-day seminar on **microprocessor applications** in instrumentation and control systems at the City University, London EC1, on September 29 and 30, 1976. Application forms from the Sira Institute Ltd, South Hill, Chislehurst, Kent BR7 5EH.

Sixty Years Ago

The following, rather untypical piece was published in *Wireless World* for August 1916. Technological prophecies seem to become fact rather quicker than the prophets imagine, but this one was a little too far-seeing. The long-wave trans-Atlantic wireless telephone service was opened on January 7th, 1927.

"According to an American scientific journal, it will not be long before England and America will be able to converse with one another by means of the wireless telephone. There are certain individuals to-day who cling to the conviction that the telephone was simply the invention of a man who had a grudge against humanity. What will they now say of the wireless telephone? There is this much to say. It will be much better than those cheap wire telephones, the wires of which are so apt to snap if you don't pay up your subscriptions. With the wireless telephone it may be that you will receive a second demand note for payment, but there will be not a man with a pair of wire-cutters in his pocket to bring the third and last demand note and cut you off if you do not pay at once. It is getting to be very exciting when we get those wireless telephones in full working order. Just imagine yourself stepping into a call box in Victoria Street and asking for "45678, Broadway, New York City." While the young lady is waking up New York you just sit down and read a few chapters from your Shakespeare or Bacon - according to which school you belong. But it will test your temper when the young lady tells you that you are through, and will you please drop three hundred and sixty-five pennies in the slot and 'turn the handle after each, please.'"